

(Multisim)¹

1. , Multisim -

2. , -

3. (,).

1.1.

, : - , - ; - ,
().

, _____ - , ,
, _____ - ,
(-) , ,
, ,
,
.

1.2.

Multisim

Multisim


()
(.1).

Sources 
(GROUND),

(POWER SOURCES),
(CONTROLLED CURRENT)

Basic (RESISTOR), (CAPACITOR), (INDUCTOR), (SWICH) Indicator

(.1.2). c

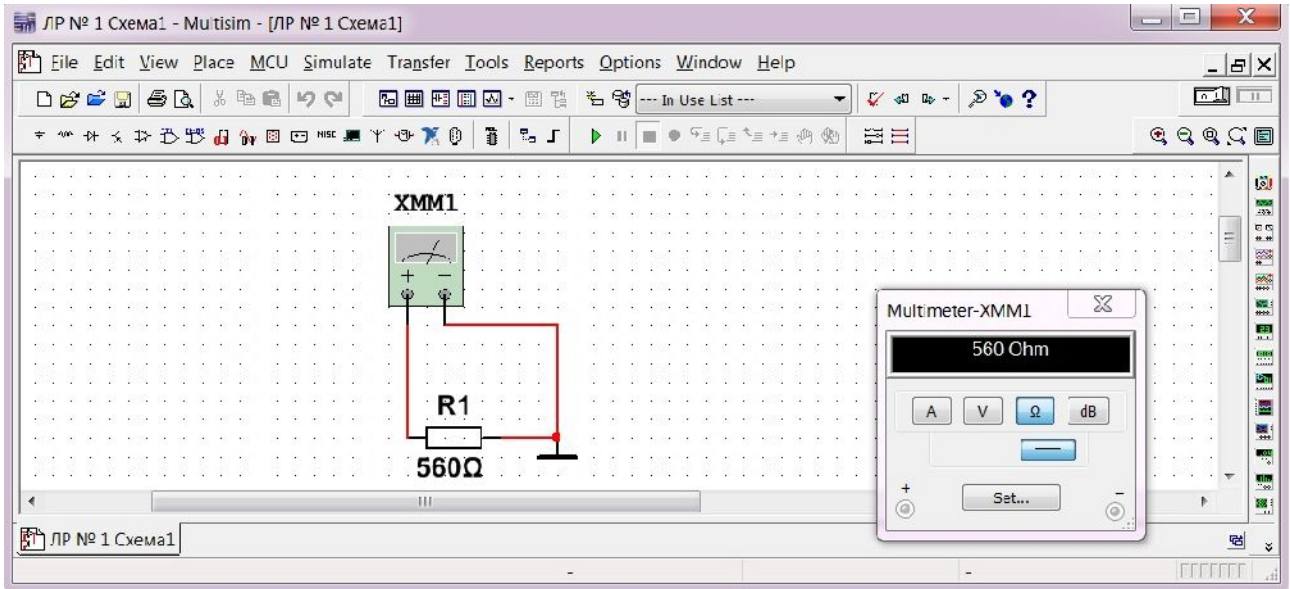
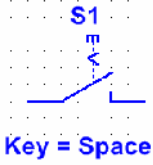

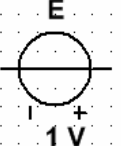

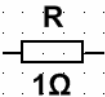

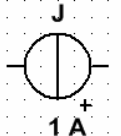
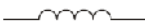


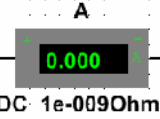

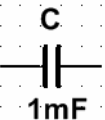




1.1 –

Multisim

«Simulation» «Run» («ON», «Stop»)



1.2 –

Multisim (standard DIN).

1.3.

(1).

1.

1.1.

1.2.

Multisim («Run»);
Multisim («Stop»).

1.1 –

R_1	$100+10 \cdot N$	
R_2	$200+10 \cdot N$	
R_3	$300+10 \cdot N$	
R_4	$400+10 \cdot N$	


($N = \dots$)

Multisim

2.

2.1.

1.3.

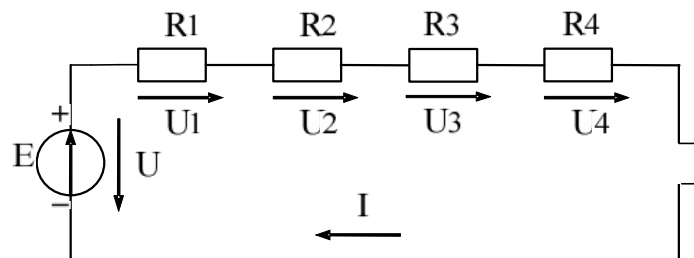

1.3 –

() .

() 1 30 .

U_1, U_2, U_3, U_4

I, U, R

2.2.

(«+» «+») .

Multisim.

Multisim (:

Tools/Capture_screene_area)

. 2 « -

».

1.2 -

	$I,$	$U,$	$U_1,$	$U_2,$	$U_3,$	$U_4,$	$R,$

2.3.

(«+») .

2.4.

Multisim

- U ;
 - U_1, U_2, U_3, U_4 R_1, R_2, R_3, R_4 .

. 1.2 « ».

2.5.

- ;
 - ;
 - , 1.1 .

. 2 « ».

2.6.

2 U « » (. 1.2).


« ».

20%,

3.

3.1.

. 1.4.

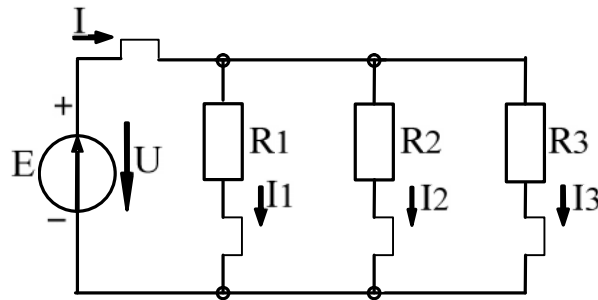

1.4 –

)

3.2.

I_1, I_2, I_3

U

I

I

2.2 - 2.4.

3

«

».

Multisim

(

:

Tools/Capture_screene_area)

1.3 –

	$U,$	$I,$	$I_1,$	$I_2,$	$I_3,$	$R,$

3.3.

R

–

$I,$

–

1.1.

1.3

«

».

3.4.

(. 1.4).

(. 1.1)

U

(. 1.3).

. 1.3


«

».

, 20%,

4. () ,
4.1.

. 1.3.

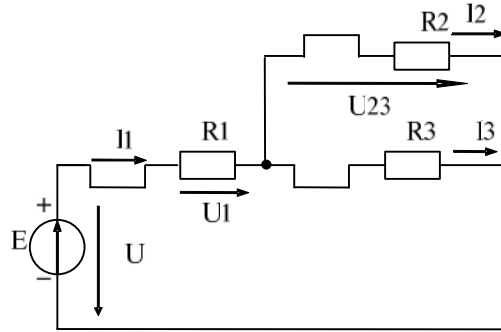

1.3 –

, U , U_1, U_2, U_3 , I_1, I_2, I_3 -
4.2. R_e , U , I_1, I_2, I_3 , U_1, U_{23} -
Multisim (:

Tools/Capture_screene_area)

. 1.4 « ».

1.4 –

	$U,$	$U_1,$	$U_{23},$	$I_1,$	$I_2,$	$I_3,$	$R,$

4.3. , R , -
 I ,

. 1.4 « ».

4.4. (. 1.1) U . 4 « -
(. 1.4). ».

, 20%,

5.

:

5.1.

$$U \quad (1.2).$$

(1.1)

$$I = \frac{E}{R},$$

$$R = R_1 + R_2 + R_3 + R_4.$$

:

$$U = IR \quad (1.2).$$

5.2.

$$U \quad (1.3).$$

(1.1)

$$I = EG,$$

$$G = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}.$$

:

$$I = UG \quad (1.3)$$

« ».

5.3.

$$U \quad (1.4).$$

(1.1)

$$I = \frac{E}{R},$$

$$R = R_1 + R_{2,3}, \quad R_{2,3} = \frac{R_2 R_3}{R_2 + R_3}.$$

:

$$I = \frac{U}{R}, \quad U = IR.$$

. 1.4 « ».

5.4.

1.

2.

3.

4.

5.

6.


7.

8.

?

9.


10.

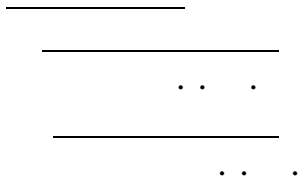


1

1.1 –

R_1	$100+10 \cdot N$	
R_2	$200+10 \cdot N$	
R_3	$300+10 \cdot N$	
R_4	$400+10 \cdot N$	

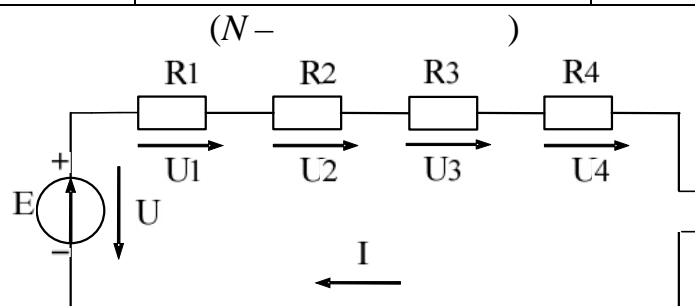


1.1 –

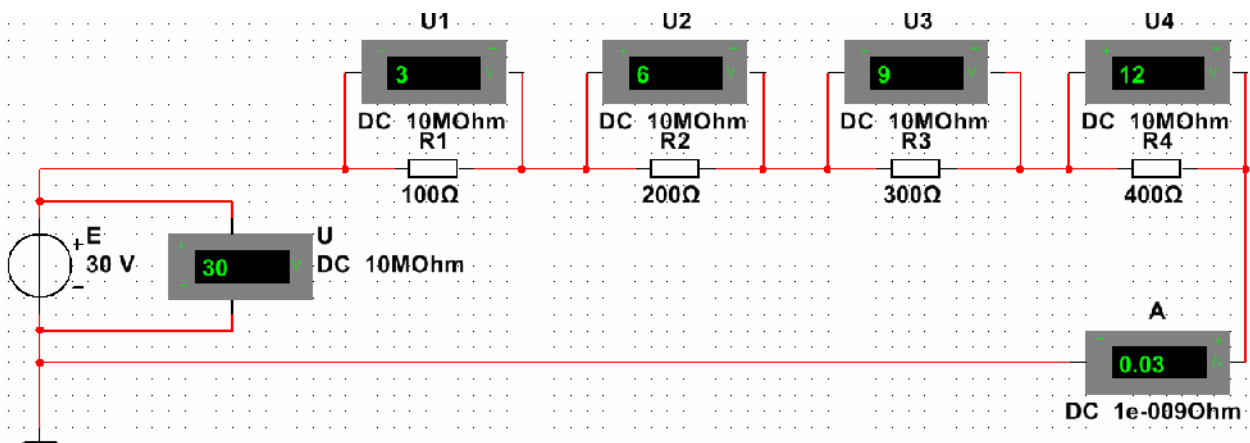


1.2 –

1.2 –

	$I,$	$U,$	$U_1,$	$U_2,$	$U_3,$	$U_4,$	$R,$

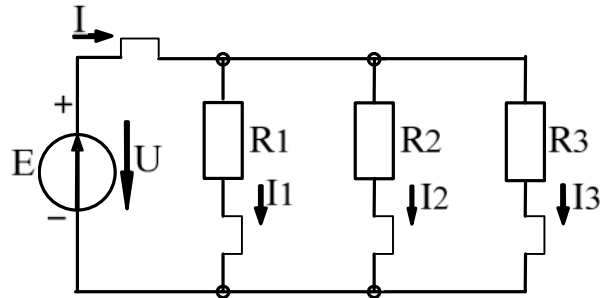


1.3 –

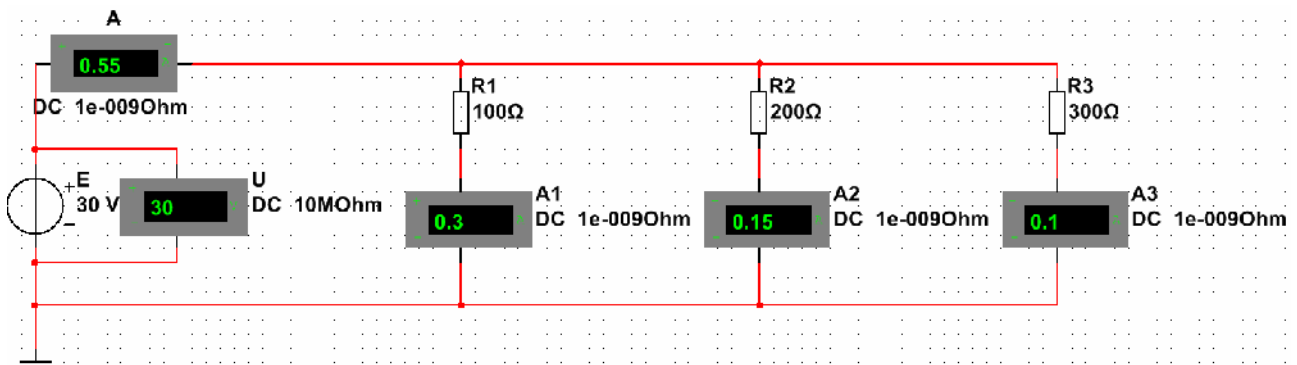

1.4 –

1.3 –

	$U,$	$I,$	$I_1,$	$I_2,$	$I_3,$	$R,$

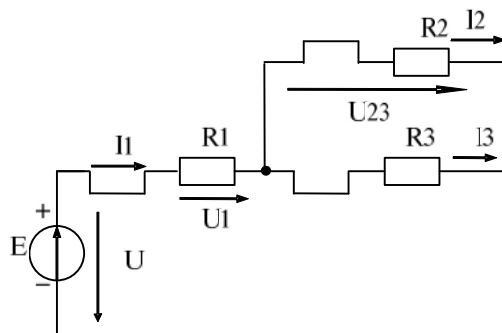

1.5 –

